

bq769x0 BMS Configurations for Cordless Appliances

Marcoo Zamora

BMS - BMP

ABSTRACT

The bq769x0 monitor family is suitable for cordless appliance battery management systems (BMS), such as robotic vacuums, due to its versatility in cell count and its high integration of features. It is often not clear how to design a BMS system due to the multitude of options and different design considerations. This document covers the basics of designing a BMS system and its related circuitry by using the bq769x0 device and presenting different examples and options for monitor configuration, protection, and the battery management controller. By selecting between the different examples, a designer will have designed a BMS schematic using the bq769x0 that can be used for 5 to 7 cell counts but the techniques can be applied to higher cell counts in the bq769x0 family.

Contents

1	Introduction	1
2	bq769x0 Monitor Configurations	2
3	Protection Configurations	7
4	Battery Management Controller Configurations	8
5	References	10

List of Figures

1	Circuit Block Diagram	2
2	5S bq76920 Configuration	3
3	6S bq76930 Configuration	4
4	7S bq76930 Configuration	4
5	5S bq76920 Configuration with External FETs	5
6	6S bq76930 Configuration With External FETs	6
7	7S bq76930 Configuration With External FETs	6
8	Low-Side Protection	7
9	bq76200 High-Side Protection	8
10	bq78350 configuration for bq76920 and bq76930	9
11	MSP430 Host Example Configuration	10

List of Tables

1	Customization Options	2
---	-----------------------------	---

1 Introduction

There is a growing trend in cordless appliances, such as robotic vacuums, to have a decrease in size, and increases in power, safety, and battery life. Because of this, it is now common to see BMS implemented into the robotic vacuum market in which battery packs typically have 5 to 7 cells.

The bq769x0 family of monitors is the optimal solution for this application due to its many benefits such as:

- Cell count scalability
- Board scalability
- ADC integration
- Coulomb counting integration
- Low power consumption
- Passive cell balancing

These many benefits help reduce potential BOM cost, increase battery life, and create a smaller solution size. While the benefits of integrating a BMS into a cordless appliance are clear, it is often not clear how to develop a BMS system. [Figure 1](#) shows an example BMS block diagram and [Table 1](#) lists all the different customization options that will be discussed for it. From this BMS system and related circuitry, the designer can then expand, modify, and customize it to suit their system needs.

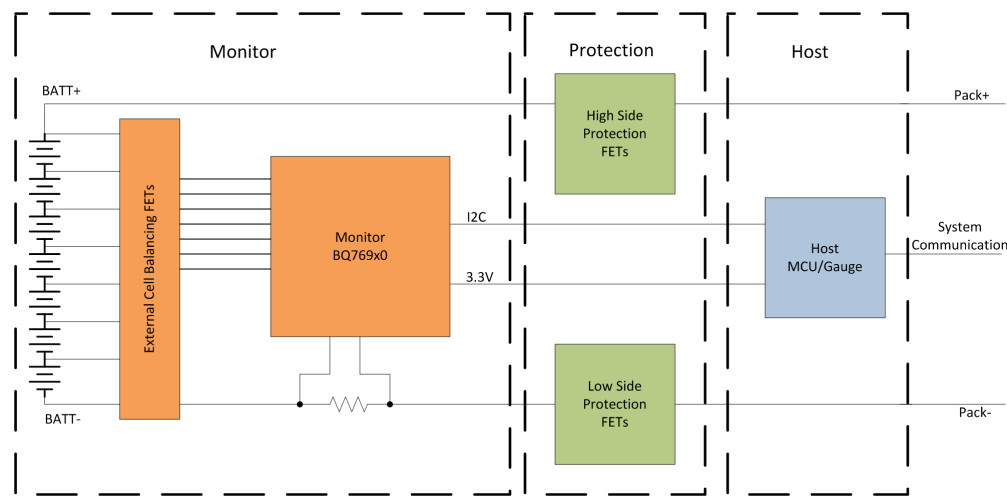


Figure 1. Circuit Block Diagram



Table 1. Customization Options

Monitor	Protection	Battery Management Controller
5S	No Protection FETs	bq78350
6S	Low-side Protection FETs using the bq769x0	MCU (MSP430 example)
7S	High-side Protection FETs using the bq76200	
5S with external FETs		
6S with external FETs		
7S with external FETs		

2 bq769x0 Monitor Configurations

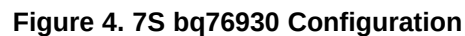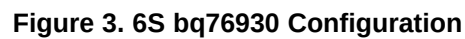2.1 bq769x0

For a BMS on a robotic vacuum, the bq769x0 monitor is a perfect fit due to its flexibility in implementation and highly integrated feature set. The integrated feature set includes ADCs and a coulomb counter which allows for rapid prototyping due to the reduced passive component count and ease of use. One of the biggest benefits of the bq769x0 family is its low power consumption which is due to the enabling and disabling of sub-blocks within the IC. In this section, there are examples of different cell configurations using the bq769x0 family to help with the design process. Aside from choosing the different cell count, it is necessary to scale the sense resistance value between pin SRP and SRN according to the required current thresholds.



2.4 External Cell Balancing

To speed up the cell balancing process, it is possible to implement external cell-balancing FETs on the bq769x0. For example, when using the bq78350 to control cell balancing, cell balancing activates during the charge phase of the cell. With a higher cell balancing current by using external FETs, the batteries will be able to recover from cell imbalance in less charge cycles. [Figure 5](#), [Figure 6](#), and [Figure 7](#) are examples of 5S, 6S, and 7S configurations using external FETs for cell balancing. For additional information regarding external cell balancing, see [SLUA749](#), section 4.

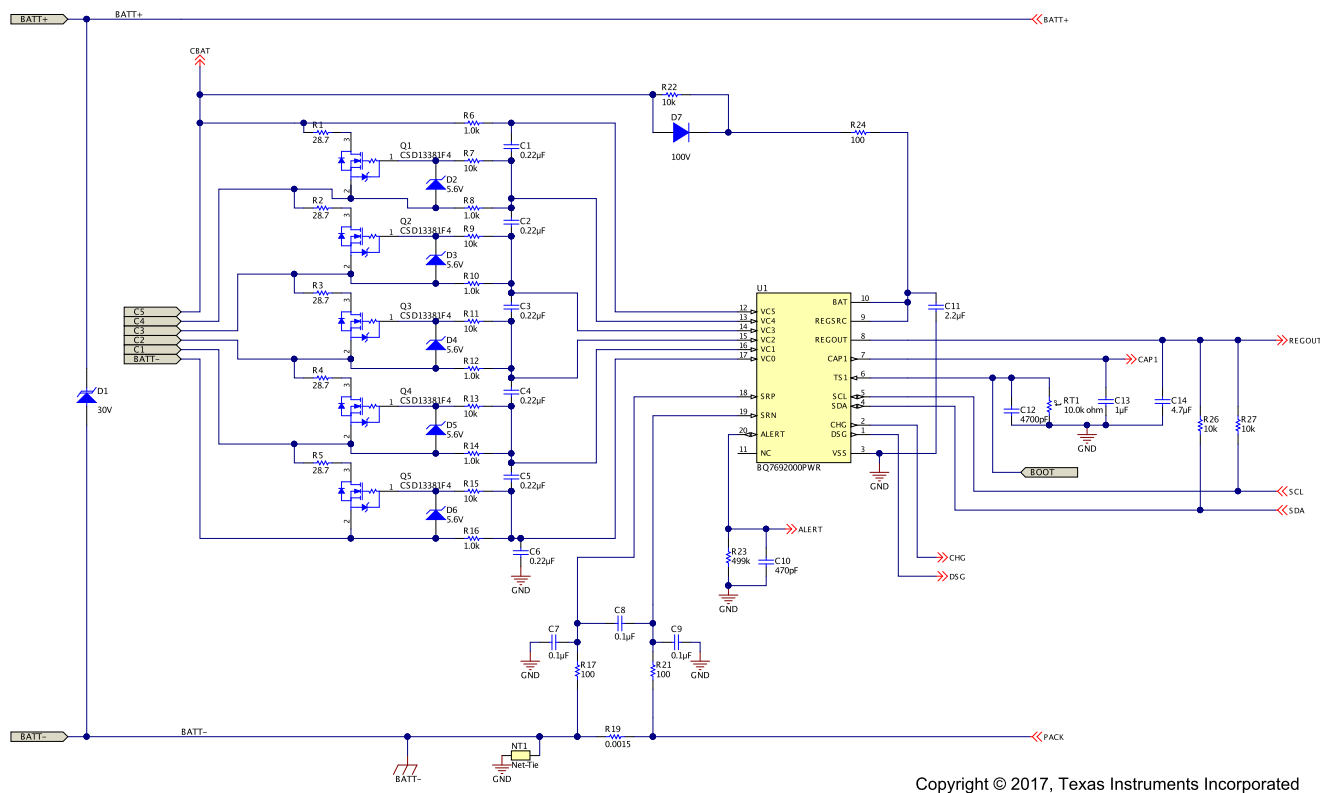


Figure 5. 5S bq76920 Configuration with External FETs



3 Protection Configurations

A bq769x0 can act as a monitor only, in which case a separate protection solution should be implemented, or it can drive low-side protection FETs directly or high-side protection FETs with the bq76200.

3.1 No Protection FETs

When a system design does not require the low-side nFET driver feature of the bq769x0, it is possible to leave the CHG and DSG pins floating and use the bq769x0 solely as a monitor. In this case, the nets BATT+ and PACK in the protection [Figure 2](#) to [Figure 7](#) become their respective exit terminals. This occurs in systems where the battery management controller is integrated with the system MCU.

3.2 Low-Side Protection FETs Using the bq769x0

By taking full advantage of the integrated low-side FET drivers in the bq769x0, it is simple to implement low-side protection, as shown in [Figure 8](#). The main design process is covered in Section 8.2.2.1 of the data sheet. The bq769x0 also has the capability to drive parallel protection FETs for increased current capability. It is important to understand that when the FETs are off in low-side protection, the battery GND and system GND are not electrically connected, which can disrupt system communication. In integrated systems where the system side is also using the battery GND this might not be an issue, but to do this in systems with replaceable battery packs, it might require an exposed GND connection.


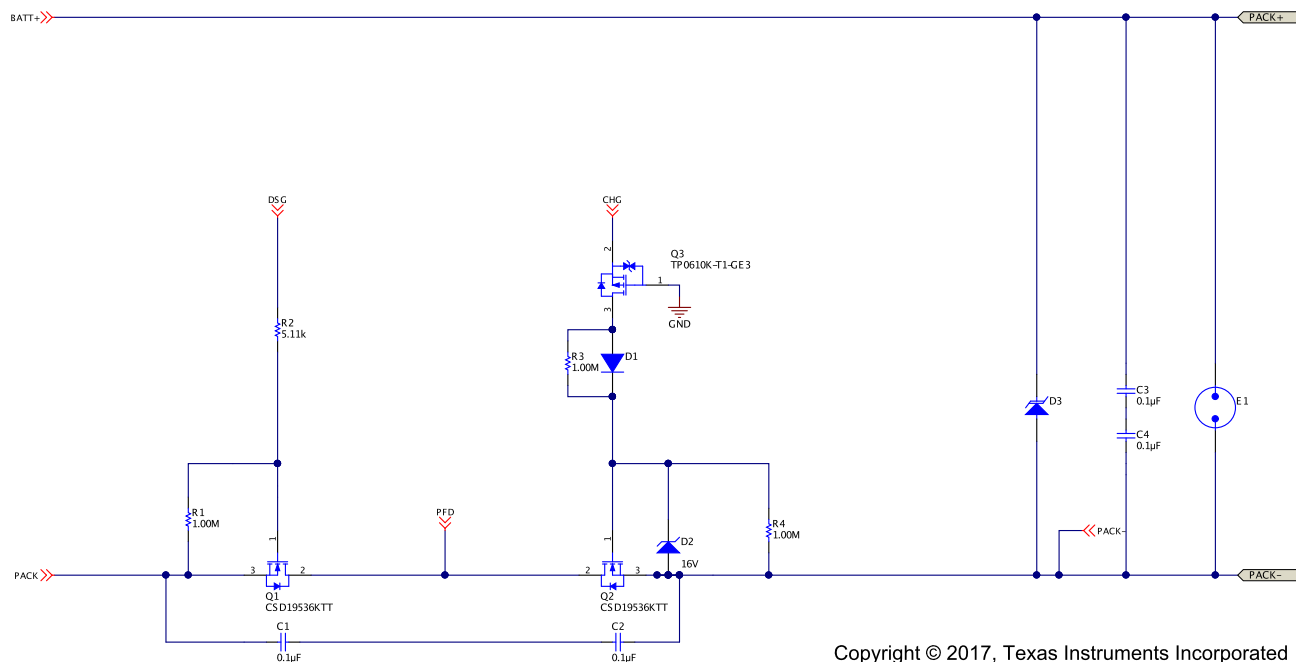


Figure 8. Low-Side Protection

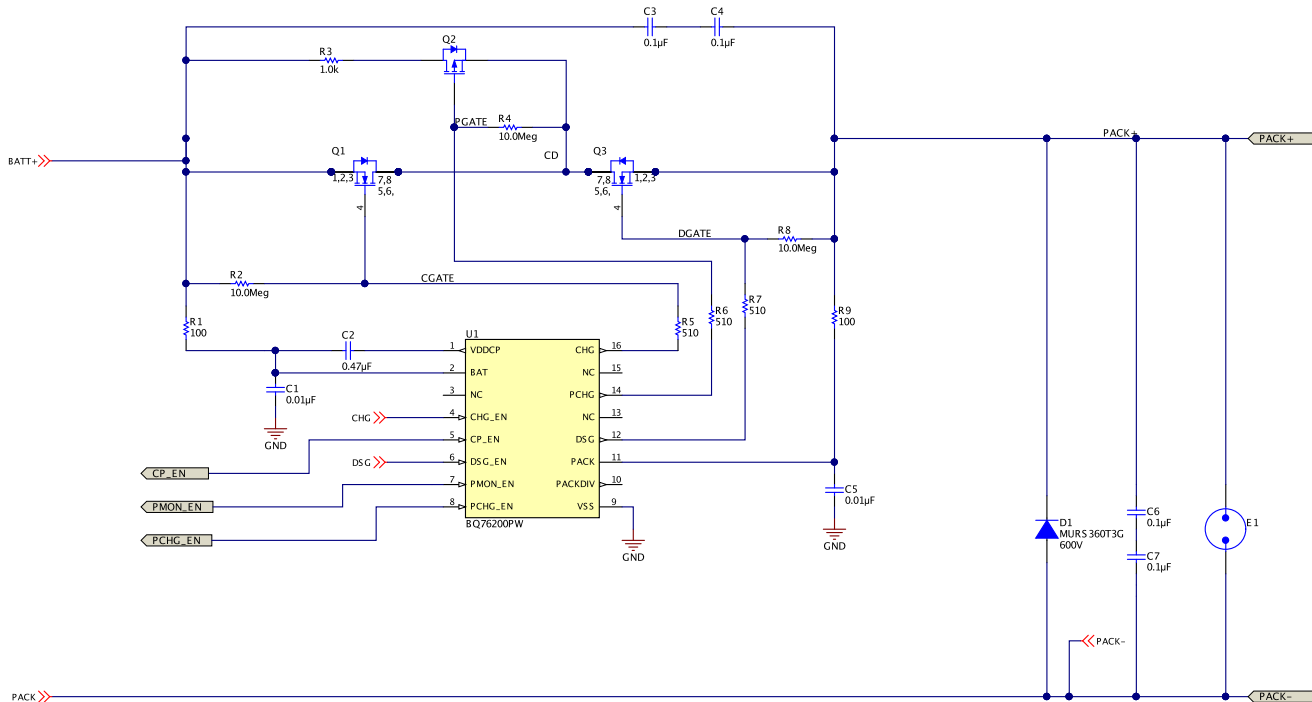3.3 High-Side Protection FETs Using the bq76200

When using the bq76200 in conjunction with the bq769x0, it is possible to have a low power, high-side, nFET protection system. The main benefit that high-side protection has over low-side protection is the lack of GND disconnection between the system and the host MCU and prevents any leakage path to comm when protected. In low-side protection there is the potential problem if PACK+ or PACK- is shorted, as it will bypass the protection features which can damage the system or the pack cells. High-side protection does not have this problem as there is no disconnect between BATT-, GND, and PACK- regardless of

the protection state which allows a common ground with the system. Figure 9 shows the high-side nFET implementation of the bq769x0 using the bq76200. This bq76200 example also implements pre-charge for heavily discharged cells by providing an alternative low current path for charging the cells. The CP_EN, PMON_EN, and PCHG_EN are enables that can either be tied to a pull up to stay enabled or to a gauge or MCU for control.



Copyright © 2017, Texas Instruments Incorporated

Figure 9. bq76200 High-Side Protection

4 Battery Management Controller Configurations

The bq769x0 monitor family communicates via I²C to a host which handles the battery management controller functions such as system-on-chip (SoC) calculation and cell balancing control. A host is necessary for the bq769x0 monitor family because the bq769x0 cannot recover from faults without host intervention. A host can also implement features such as battery fuel gauge, and low-side pre-charge when low-side protection is in use. By using the integrated coulomb counter of the bq769x0, a host can add additional protection features such as charge overcurrent protection (OCC).

4.1 bq78350 Gauge Example Configuration

For the bq769x0 devices, TI offers the bq78350-R1 gas gauge and battery management controller to simplify the process of implementing a host. The bq78350-R1 offers a wide array of features such as accurate fuel gauging, LED and LCD indication driver, state-of-health (SoH) monitor, cell balancing, fault recovery, along with additional primary- and secondary-protection features. All these features can be programmed into non-volatile memory in the bq78350-R1 by using SMBus which minimizes any programming required on the user side. The system-side communication of this device is limited to SMBus. Example configurations for the bq78350 communicating with the bq76920 and bq76930 are shown in Figure 10.


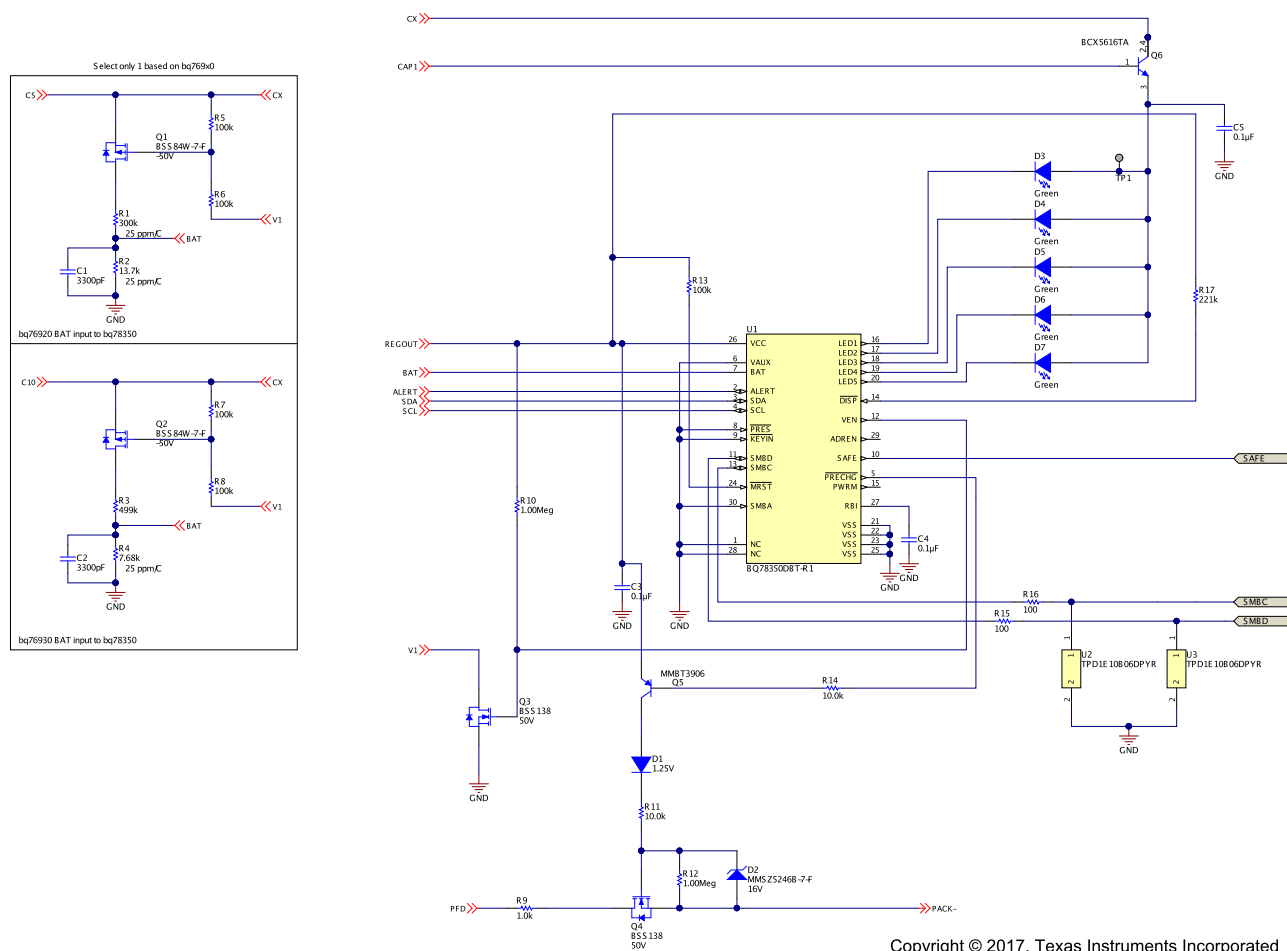


Figure 10. bq78350 configuration for bq76920 and bq76930

 4.2 Host MCU MSP430 Example Configuration

An alternative to the bq78350 is an MCU, such as the MSP430, as the battery management controller. A host MCU offers system flexibility in situations that the bq78350-R1 fixed feature set cannot meet. An example in MCU flexibility is the system side communication protocols such as in [Figure 11](#) from [TIDA-00449](#), where the main system communication out of the MCU is UART. A unique flexibility an MCU has is that an MCU is also able to be programed as a protection FET controller in systems where the bq769x0 is acting solely as a monitor.



5 References

- *bq769x0 3-Series Cell Battery Monitor Family for Li-Ion and Phosphate Applications data sheet* ([SLUSBK2](#))
- *bq76930 and bq76940 Evaluation Module* ([SLVU925](#))
- *bq76920 Evaluation Module User's Guide* ([SLVU924](#))
- *10s Battery Pack Monitoring, Balancing, and Comprehensive Protection, 50-A Discharge Reference Design* ([TIDUAR8](#))
- *bq769x0 Family Top 10 Design Considerations* ([SLUA749](#))
- *bq769x0 Boot Switch Alternatives* ([SLUA769](#))
- *bq78350-R1 CEDV Li-Ion Gas Gauge and Battery Management Controller Companion to the bq769x0 Battery Monitoring AFE* ([SLUSCD0](#))
- *bq76200 High Voltage Battery Pack Front-End Charge/Discharge High-Side NFET Driver* ([SLUSC16](#))
- *bq76200 Beyond the Simple Application Schematic* ([SLUA794](#))

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated